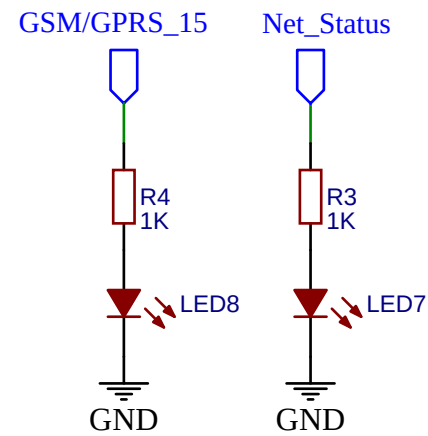


STATUS LED's

GSM/GPRS_15

Net_Status

The image shows two circuit diagrams for status LEDs. The first diagram, labeled 'GSM/GPRS_15', shows a green wire connected to a blue pentagon-shaped component, which is then connected to a red resistor labeled 'R4 1K'. The other end of the resistor is connected to a red LED labeled 'LED8', which is then connected to a ground symbol labeled 'GND'. The second diagram, labeled 'Net_Status', shows a similar setup with a green wire connected to a blue pentagon-shaped component, which is connected to a red resistor labeled 'R3 1K'. The other end of the resistor is connected to a red LED labeled 'LED7', which is then connected to a ground symbol labeled 'GND'.



ESP32-WROOM-32UE

U2
ESP32-WROOM-32U

3V3

C8 10uF

C2 100nF

EN

SENSOR_VP

SENSOR_VN

IO34

IO35

IO32

IO33

IO25

IO26

IO27

IO14

IO12

GND

IO13

SD2

SD3

CMD

CLK

SD0

SD1

IO15

IO2

GND

IO23

IO22

TXD0

RXD0

IO21

NC

IO19

IO18

IO5

IO17

IO16

IO4

IO0

IO2

IO23

IO22

TXD0

RXD0

IO21

NC

IO19

IO18

IO5

IO17

IO16

IO4

IO0

U0TX

U0RX

SCL_Sensor

SDA_Sensor


GPRS_TX_17

GPRS_RX_16

IO0

Relay_2

GSM/GPRS_15

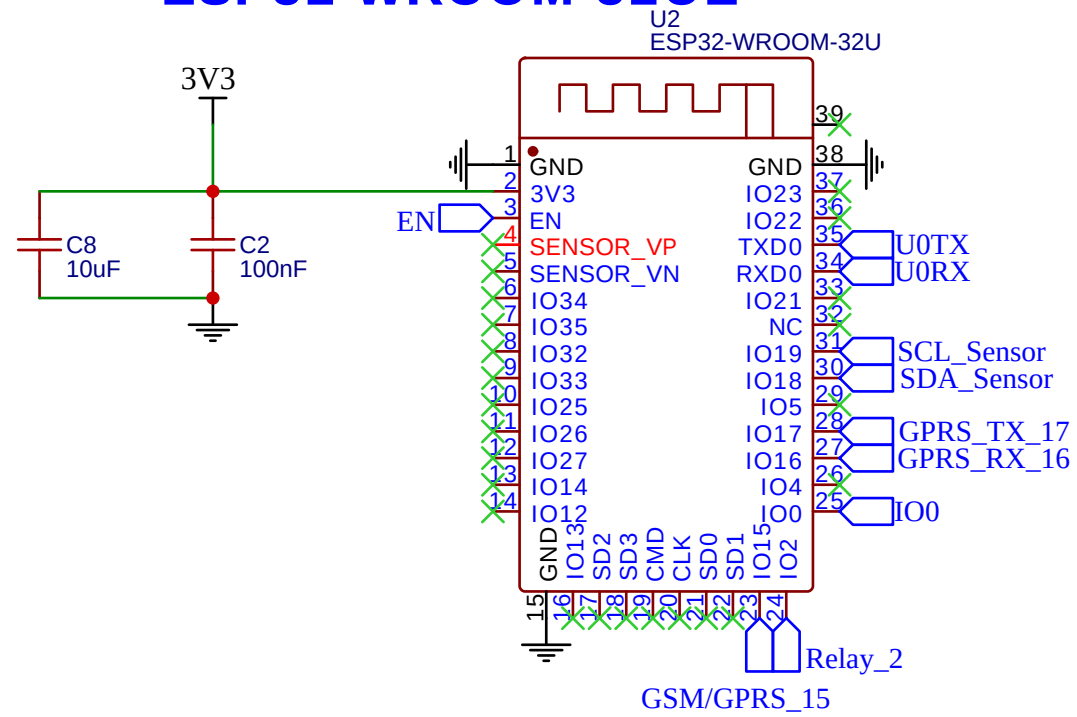

External I2C Interface

The diagram illustrates the wiring for an external I2C interface using a PH-4A RHOS connector. The connector has four pins, numbered 1 to 4. Pin 1 is connected to a 3V3 power supply. Pin 2 is connected to the SDA_Sensor. Pin 3 is connected to the SCL_Sensor. Pin 4 is connected to a GND (ground) symbol.

3V3

CN1
PH-4A RHOS

1 1

2 2


3 3

4 4

SDA_Sensor


SCL_Sensor

GND

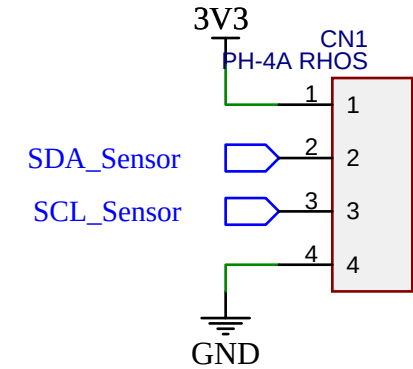


RESET and Prog PIN

The diagram illustrates the wiring for the RESET and Prog PIN. Both circuits are powered by a 3V3 supply. The RESET circuit uses resistors R19 (10K) and R13 (470) in series, with a switch EN connected to the 3V3 supply and the junction of R19 and R13. The Prog PIN circuit uses resistors R16 (10K) and R11 (470) in series, with a switch IO0 connected to the 3V3 supply and the junction of R16 and R11. Both circuits include a TS-1088R-02026 switch (SW6 for RESET, SW5 for Prog PIN) connected to the junction of the resistors and ground (GND).

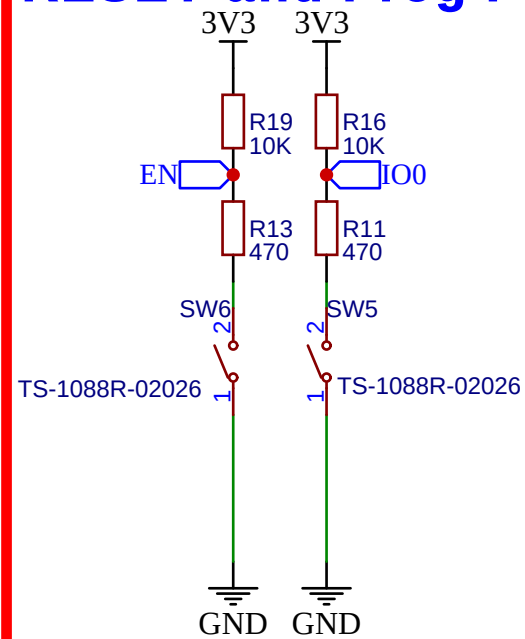

BH1750 Light Sensor

The diagram illustrates the wiring for a BH1750 Light Sensor module. The sensor, labeled U6 (BH1750FVI-TR), is connected to a 3V3 power supply. The VCC pin (pin 1) is connected to the 3V3 supply through a 10K pull-up resistor (R10). The ADDR pin (pin 2) is connected to GND. The SCL pin (pin 3) is connected to the 3V3 supply through a 4.7K pull-up resistor (R2). The SDA pin (pin 4) is connected to the 3V3 supply through a 4.7K pull-up resistor (R1). The sensor's output is connected to a 3V3 supply through a 1K resistor (R22). The sensor's output is connected to a 3V3 supply through a 1K resistor (R22). The sensor's output is connected to a 3V3 supply through a 1K resistor (R22).

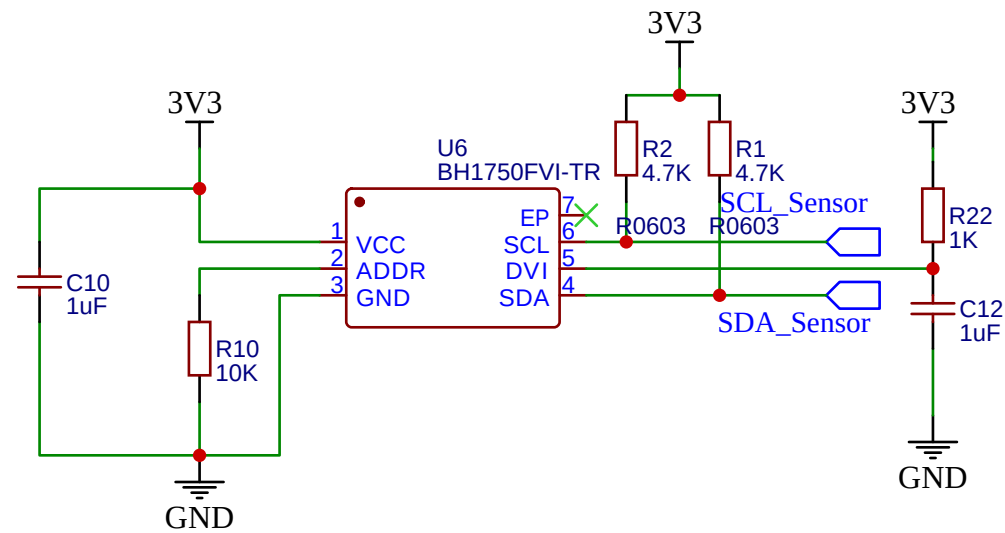

UART Programming Pins

3V3


U0RX

U0TX


GND

1 2 3 4


CN2
PH-4A RHOS

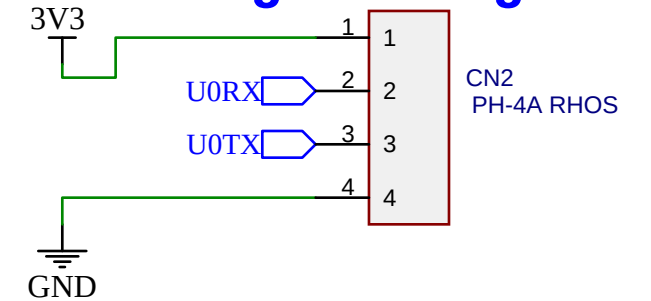



AC to 5V including AC On/Off Relay

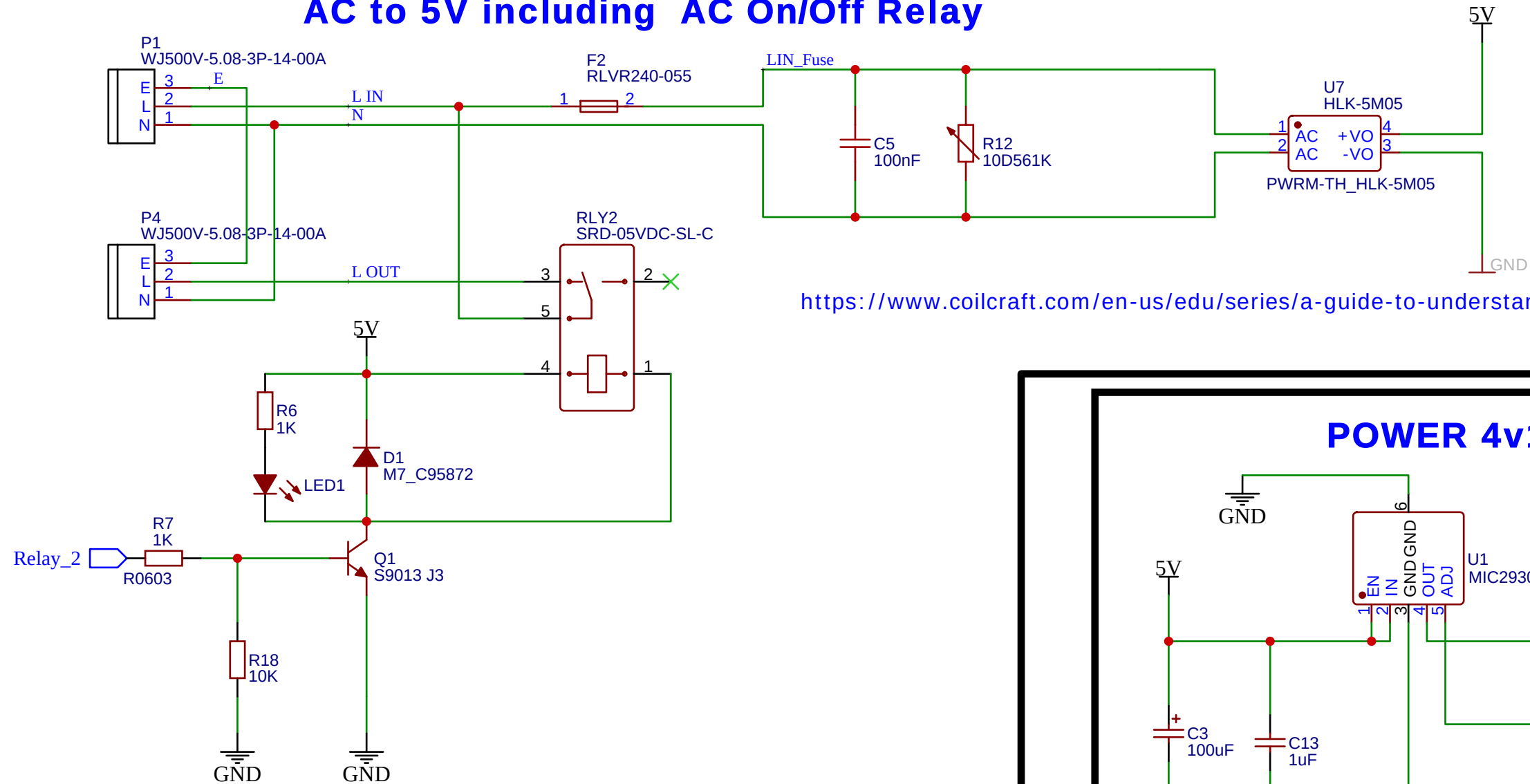

POWER 4v1 SIM800L

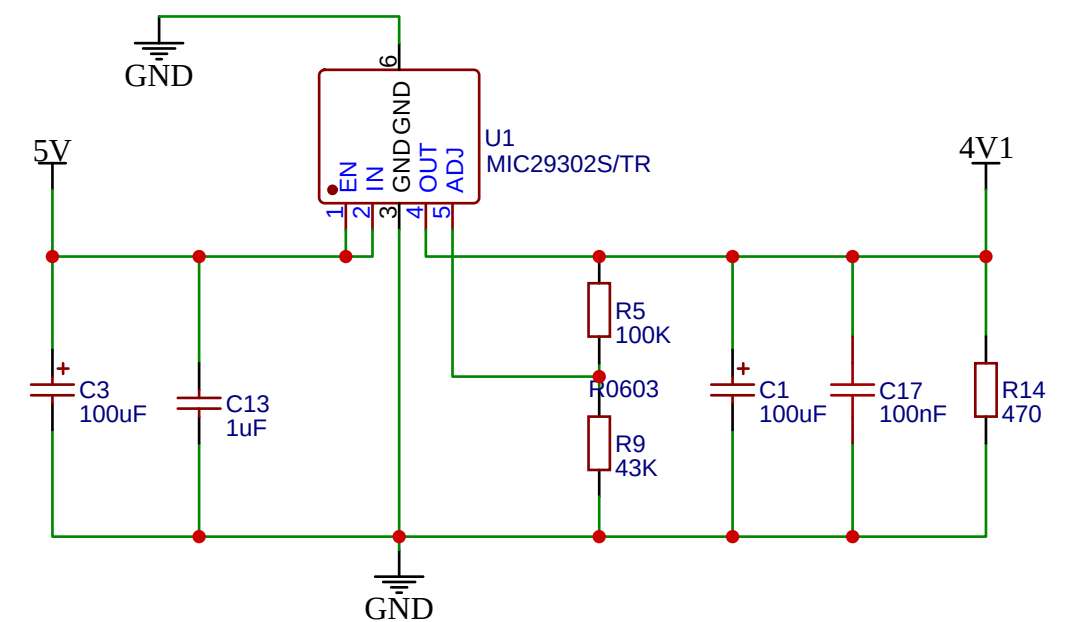

POWER 3v3 ESP32

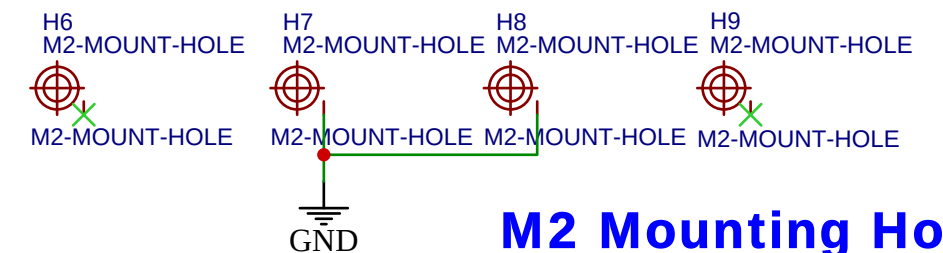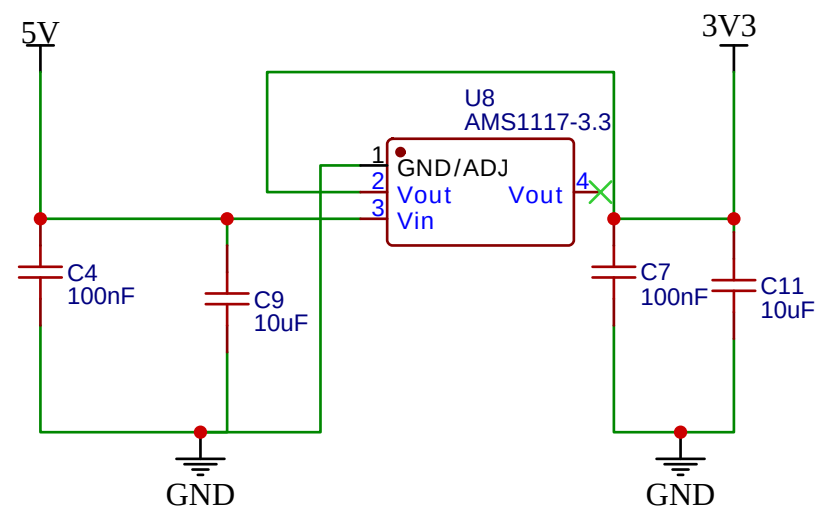

M2 Mounting Hole

TITLE: POWER		REV: 1.0
EasyEDA	Company: Your Company	Sheet: 1/2
	Date: 2021-08-31	Drawn By: caoilte donohoe

GPRS SIM800C with SIM Card and ESD protection

